

1. CMOS



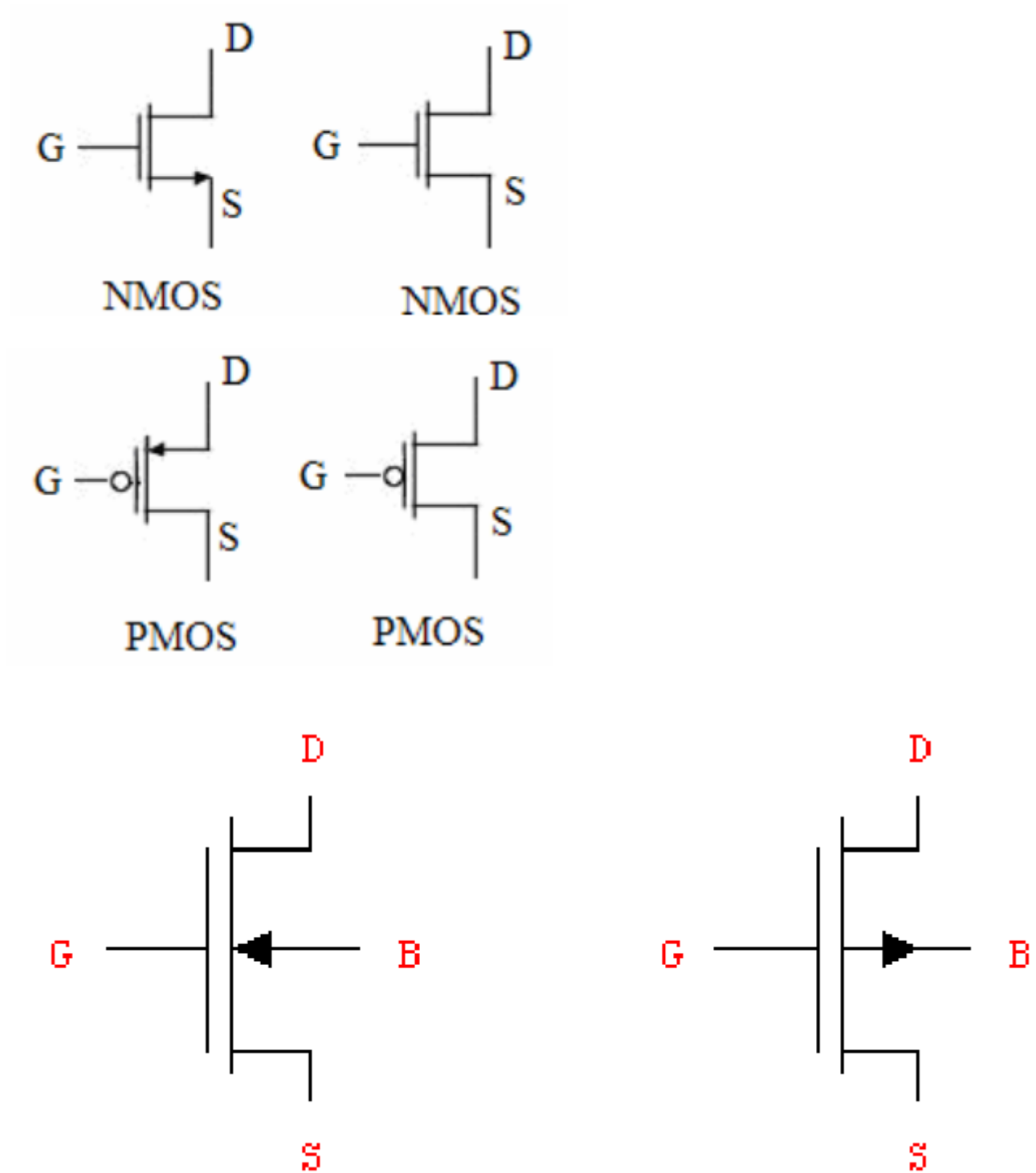


Fig 1.2.1 NMOS and PMOS (from left to right) schematic symbol

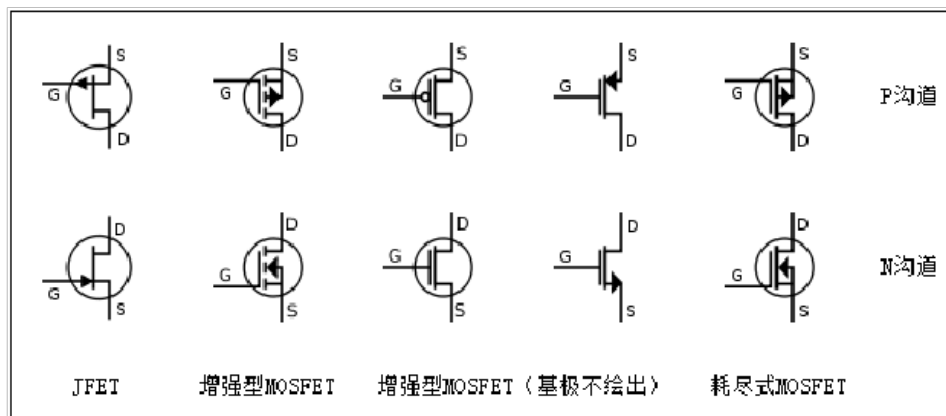


数字电路用的都是增强型, G级有圈表示PMOS 反之NMOS

1.1 INV

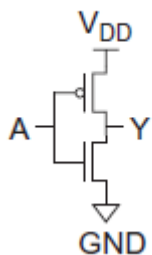

1.2 NAND

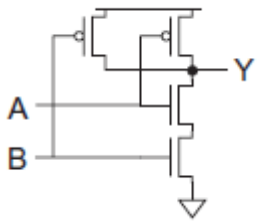

1.3 NOR

