

1. CMOS

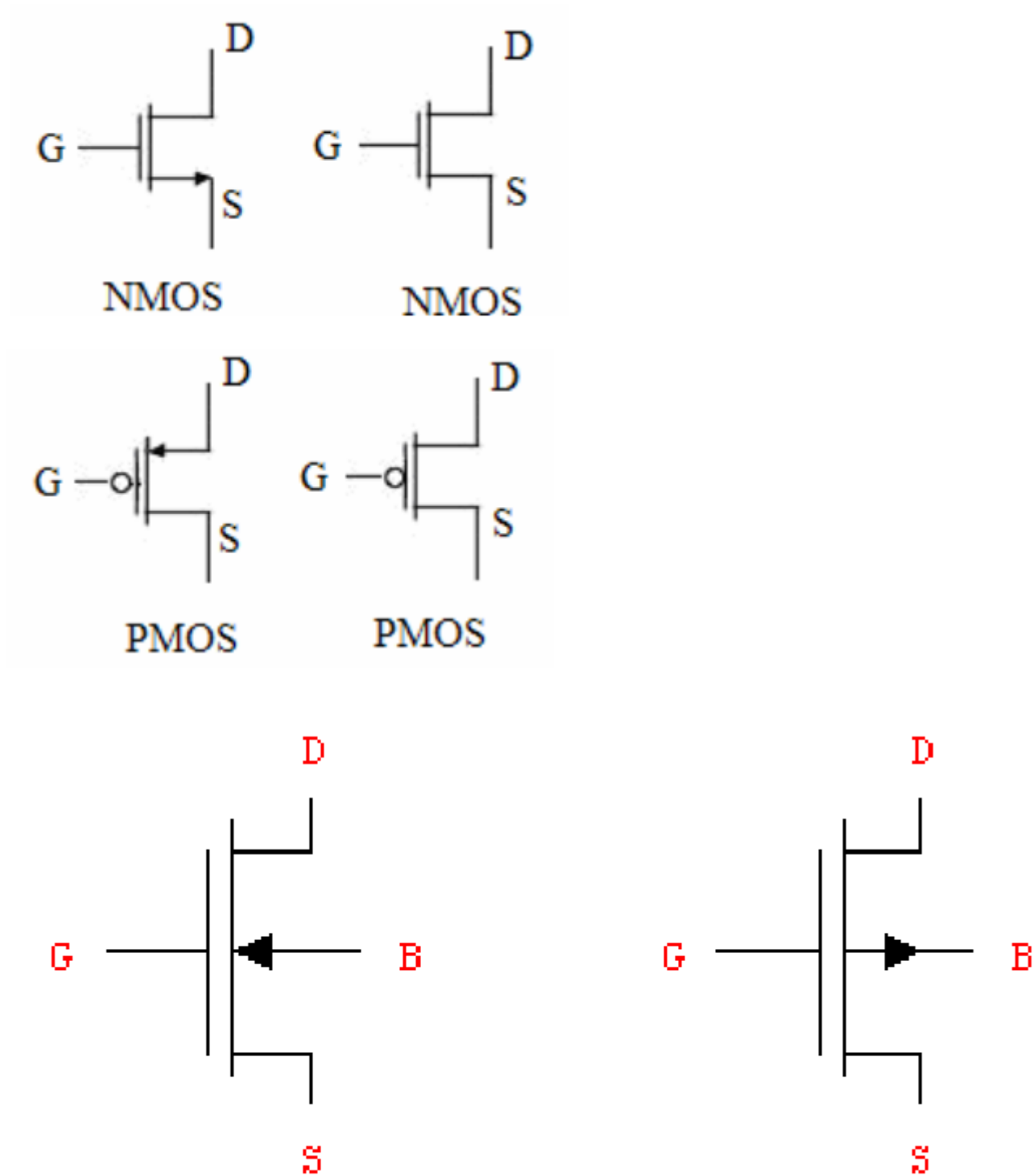


Fig 1.2.1 NMOS and PMOS (from left to right) schematic symbol

1.1 invert

