

# 1. datapath


## 1.1 pipeline

有三种pipeline, 这三种pipe从端口上来看时序是一样的, 最终效果都是用正沿打一拍

### Receiver1xPipeline


前一级是用正沿打出来的, 这里先用负沿打一下是为了修hold 比如前级reg的clk tree比较短, 后级的clk tree比较长, 这样后级采样的时候hold容易出问题。

Receiver1xPipeline

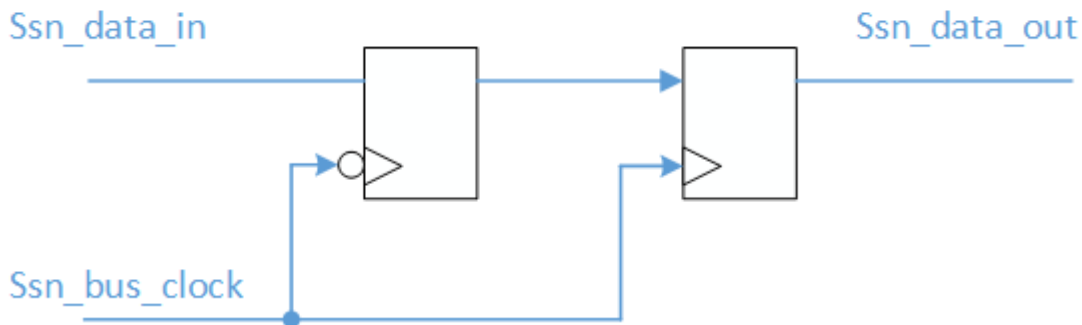


### Pipeline

Pipeline

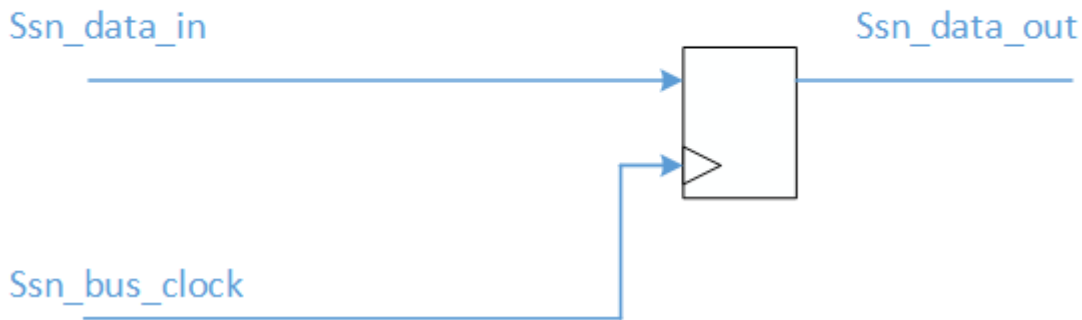


### OutputPipeline

### OutputPipeline

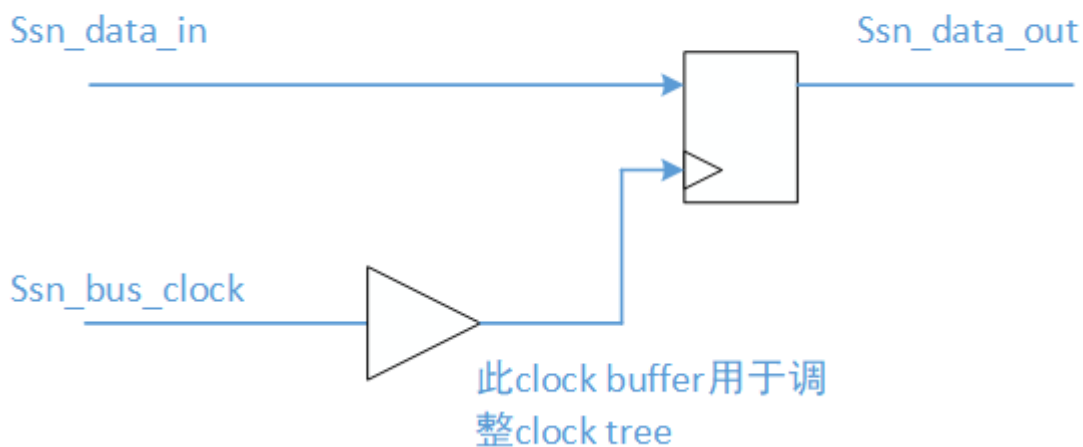

### RxPipeline

#### ReceiverPipeline 定制

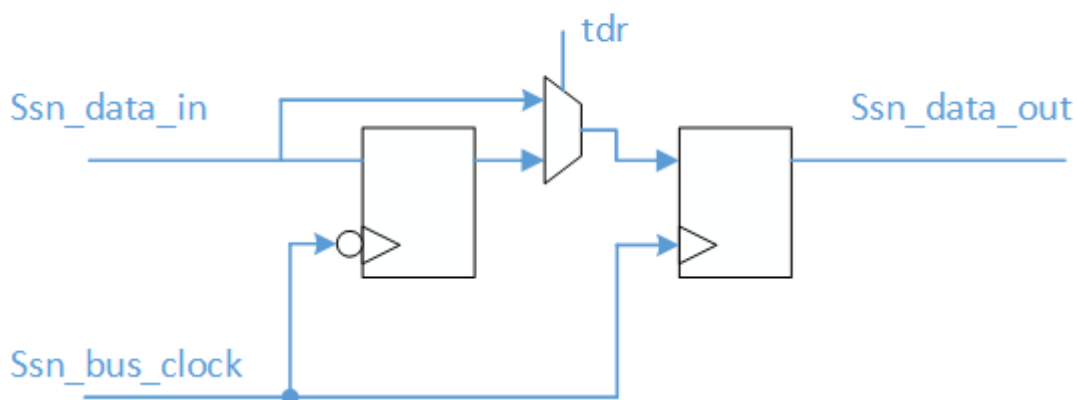

## 1.2 example 1

```
DataPath(1) {
  output_bus_width      : 2;
  Pipeline(2) {
  }
  ScanHost(1) {
  }
  Pipeline(1) {
  }
}
```

graph LR
 ssn\_busin-->pipe1
 pipe1-->ssh
 ssh-->pipe2
 pipe2-->ssn\_busout

## 1.3 example

```

DataPath(1) {
  output_bus_width      : 2;
  Pipeline(2) {
  }
  ScanHost(1) {
  }
  Multiplexer(1) {
    Connections {
      secondary_bus_data_in : ssn_s0_bus_data_in[1:0];
    }
  }
  Pipeline(1) {
    ExtraOutputPath {
      Connections {
        bus_clock_out      : ssn_s0_bus_clock_out;
        bus_data_out       : ssn_s0_bus_data_out[1:0];
      }
    }
  }
}

```

graph LR
 ssn\_busin-->pipe1
 pipe1-->mux1
 pipe1-->ssn\_s0\_bus\_data\_out
 ssn\_s0\_bus\_data\_out -.->ssn\_s0
 ssn\_s0-->mux1
 mux1-->ssh
 ssh-->pipe2
 pipe2-->ssn\_busout

## 1.4 example

```

DataPath(1) {
  output_bus_width      : 2;
  ScanHost(1) {
  }
  Multiplexer(2) {
    Connections {
      secondary_bus_data_in : ssn_s1_bus_data_in[1:0];
    }
  }
  Pipeline(2) {
    ExtraOutputPath {
      Connections {
        bus_clock_out      : ssn_s1_bus_clock_out;
        bus_data_out       : ssn_s1_bus_data_out[1:0];
      }
    }
  }
  Multiplexer(1) {
    Connections {
      secondary_bus_data_in : ssn_s0_bus_data_in[1:0];
    }
  }
}

```

```

    }
  }
  Pipeline(1) {
    ExtraOutputPath {
      Connections {
        bus_clock_out      : ssn_s0_bus_clock_out;
        bus_data_out       : ssn_s0_bus_data_out[1:0];
      }
    }
  }
}

```

```

graph LR
  ssn_busin-->pipe1
  pipe1-->mux1
  pipe1-->ssn_s0_bus_o
  ssn_s0_bus_o -.->ssn_s0
  ssn_s0-->mux1
  mux1-->pipe2
  pipe2-->mux2
  pipe2-->ssn_s1_bus_o
  ssn_s1_bus_o -.->ssn_s1
  ssn_s1-->mux2
  mux2-->ssh
  ssh-->ssn_busout

```

## 1.5 example

```

DataPath(1) {
  output_bus_width      : 2;
  Pipeline(8) {
  }
  ScanHost(1) {
    OnChipCompareMode {
    }
  }
  Multiplexer(1) {
    Connections {
      secondary_bus_data_in : ssn_s0_bus_data_in[1:0];
    }
    Pipeline(22) {
    }
  }
  Pipeline(1) {
    ExtraOutputPath {
      Connections {
        bus_clock_out      : ssn_s0_bus_clock_out;
        bus_data_out       : ssn_s0_bus_data_out[1:0];
      }
    }
  }
}

```

```

graph LR
  ssn_busin-->pipe1
  pipe1-->mux1
  pipe1-->ssn_s0_bus_o
  ssn_s0_bus_o -.->ssn_s0
  ssn_s0-->pipe22
  pipe22-->mux1
  mux1-->ssh
  ssh-->pipe8
  pipe8-->ssn_busout

```

## 1.6 example

```

DataPath(1) {
  output_bus_width      : 2;
  Pipeline(8) {
  }
  ScanHost(1) {
    OnChipCompareMode {
    }
  }
  Multiplexer(1) {
    Connections {
      secondary_bus_data_in : ssn_s0_bus_data_in[1:0];
    }
    Pipeline(22) {
    }
  }
  Pipeline(1) {
    ExtraOutputPath {
      Connections {
        bus_clock_out      : ssn_s0_bus_clock_out;
        bus_data_out       : ssn_s0_bus_data_out[1:0];
      }
      Pipeline(11) {
      }
    }
  }
}

```

graph LR
 ssn\_busin-->pipe1
 pipe1-->mux1
 pipe1-->pipe11
 pipe11-->ssn\_s0\_bus\_o
 ssn\_s0\_bus\_o -.->ssn\_s0
 ssn\_s0-->pipe22
 pipe22-->mux1
 mux1-->ssh
 ssh-->pipe8
 pipe8-->ssn\_busout